

CSE 3203 CT 4 Assignment
Roll No: 1803034

Assignment Problem:

Build CPU based on following requirements:

1. Word Size of CPU = 4 bit
2. ALU Operations = Add, ROL , Xor
3. Register Number = 4
4. Size of RAM = 7
5. Word size of ISA and RAM = 15 bit
6. CPU Instructions = Register Mode , Immediat Mode , Jmp ,JC

Solution:

Simulator Design:

1. ALU Circuit (Top to Bottom all circuits):

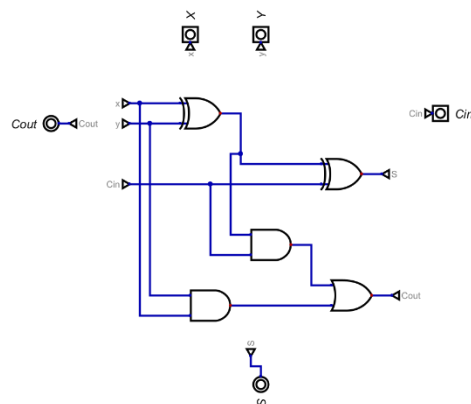


Fig: 1 bit Full Adder

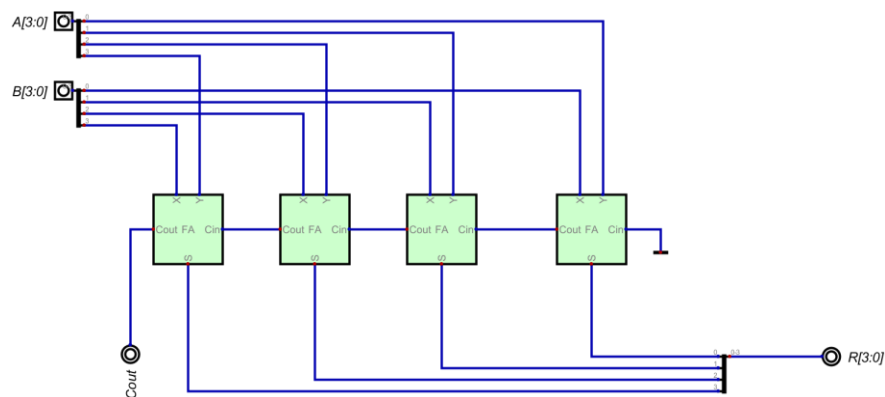


Fig: 4 bit Adder

2. Register Set Circuit (Top to Bottom all circuits):

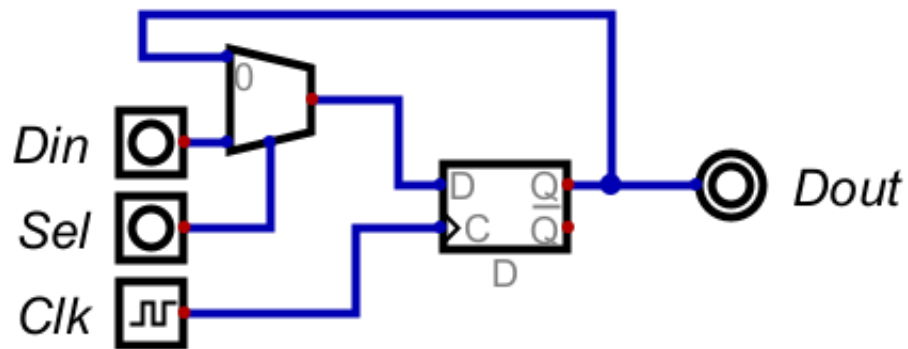


Fig: 1 bit Register

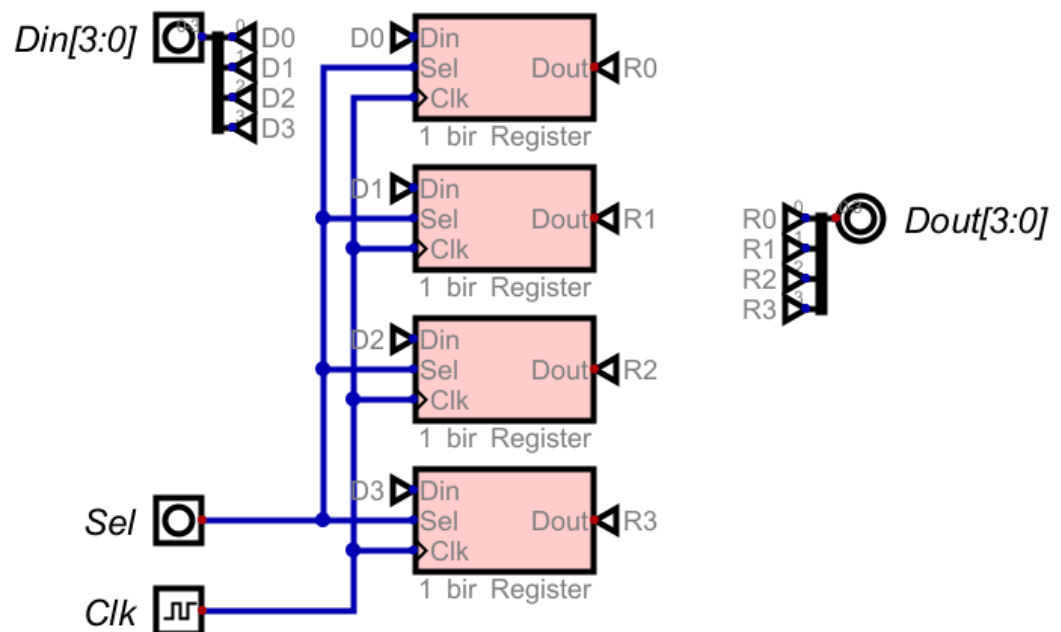


Fig: 1 x 4 Register

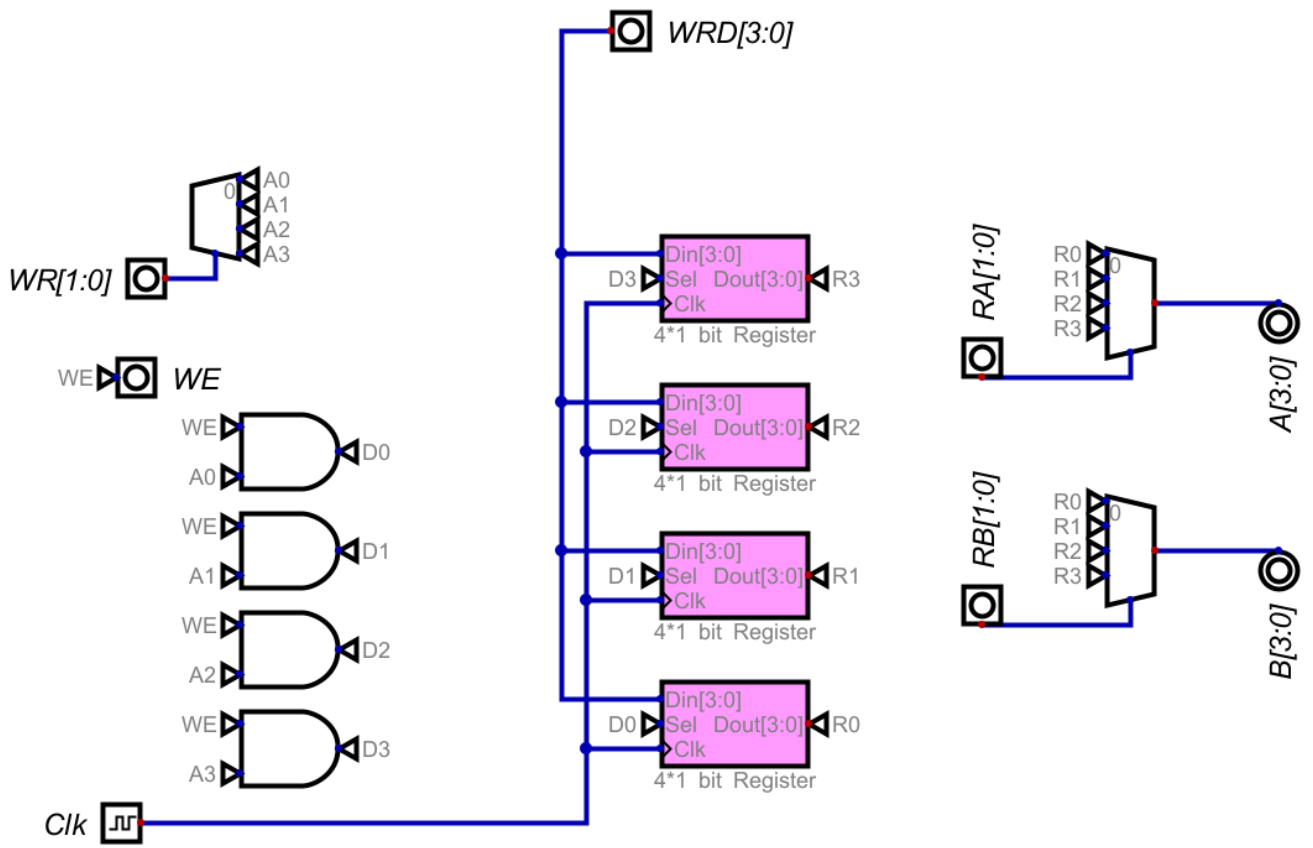


Fig: 4x4 Register Set

3. RAM Circuit (Top to Bottom all circuits):

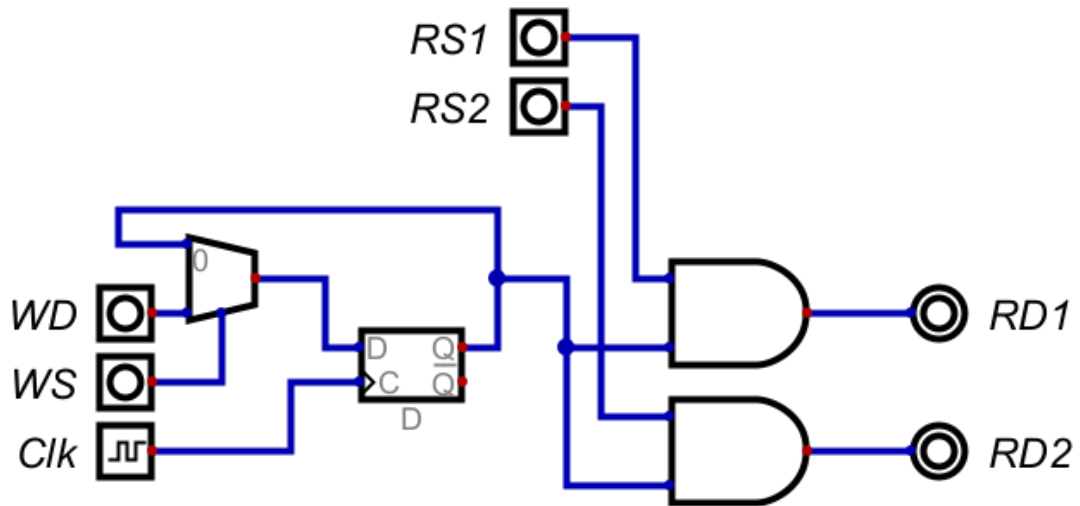


Fig: 1 x 1 RAM

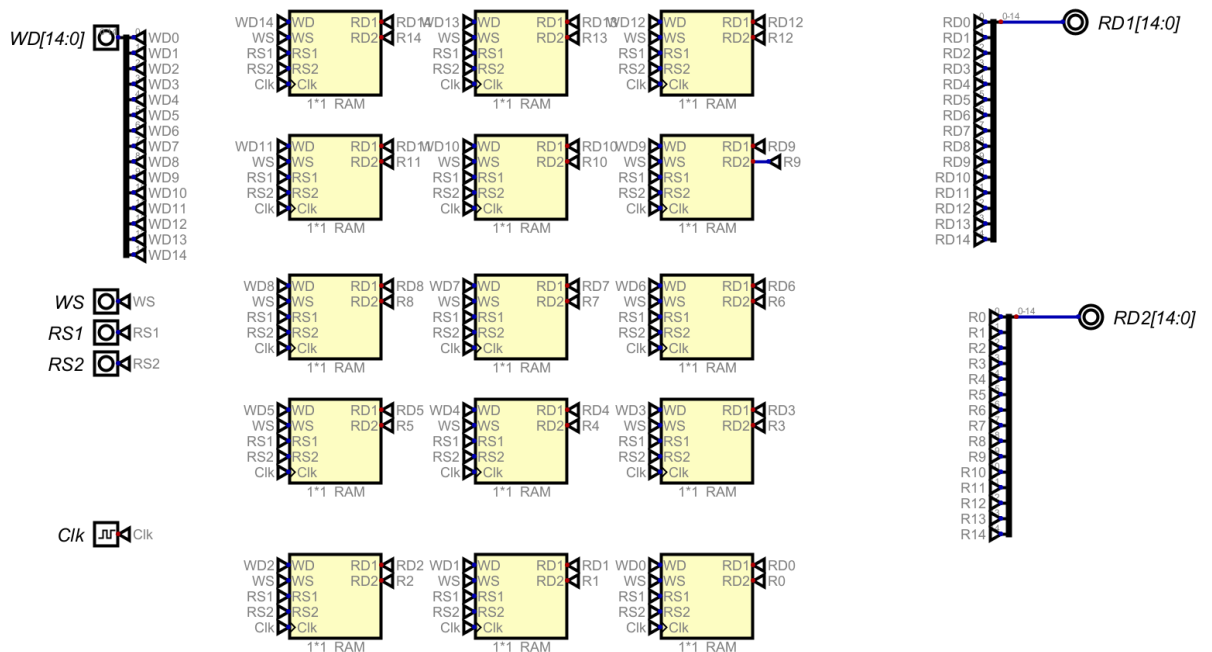


Fig: 1 x 15 RAM

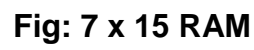


Fig: 7 x 15 RAM

4. ISA

1 st bit	2 nd bit	3 rd bit	4 th bit	5 th bit	6 th bit	7 th bit	8 th bit	9 th bit	10 th bit	11 th bit	12 th bit	13 th bit	14 th bit	15 th bit
---------------------	---------------------	---------------------	---------------------	---------------------	---------------------	---------------------	---------------------	---------------------	----------------------	----------------------	----------------------	----------------------	----------------------	----------------------

0 0 (Regular Mode)	0 0 ADD	X X Address of Register (RA)	X X Address of Register (RB)	X X X X X X X Don't Care (7 bit)						
	0 1 ROL									
	1 0 XOR									

0 1 (Immidiates Mode)	0 0 ADD	X X Address of Register (RA)	X X X X Constant (4 bit)	X X X X X Don't Care (5 bit)
	0 1 ROL			
	1 0 XOR			

<p>1 0 (Jmp Mode)</p>	<p>0 0 JC</p>	<p>X X X Address of Instruction Pointer (RA)</p>	<p>X X X X X X X X Don't Care (8 bit)</p>
---------------------------------------	-------------------------------	---	---

5. CPU (Top to Bottom all circuits):

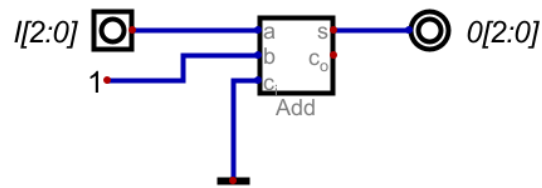


Fig : 3 bit PC Adder

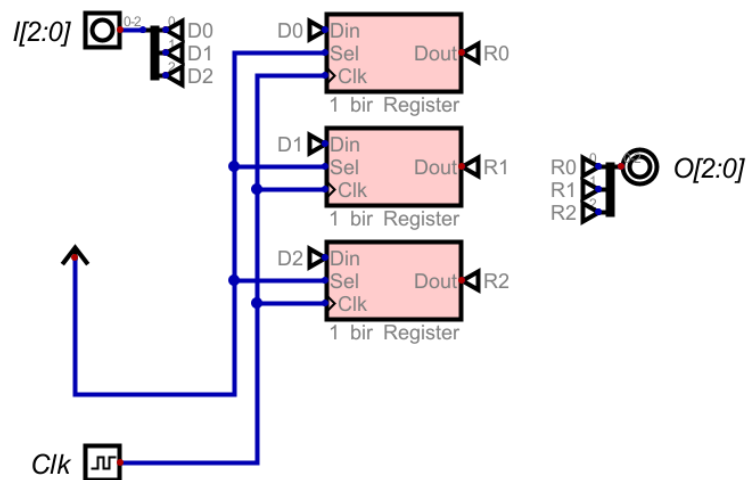


Fig: 3 bit Program Counter Register

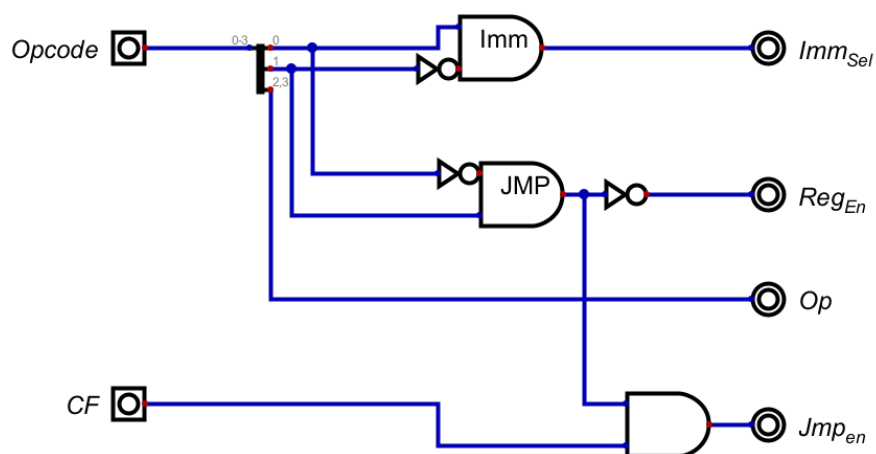


Fig: Control Unit

